

Sergio Garcia Tapia

Digital Design and Computer Architecture: RISC-V, by Sarah and David Harris

Chapter 4: Hardware Description Languages

February 23, 2024

The following exercises may be done using your favorite HDL. If you have a simulator available, test your design. Print the waveforms and explain how they prove that it works. If you have a synthesizer available, synthesize your code. Print the generated circuit diagram, and explain why it matches your expectations.

Exercise 4.1. Sketch a schematic of the circuit described by the following HDL code. Simplify the schematic so that it shows a minimum number of gates.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exercise1 is
    port(a, b, c: in STD_LOGIC;
         y, z: out STD_LOGIC);
end;

architecture synth of exercise1 is
begin
    y <= (a and b and c) or (a and b and not c) or (a and not b and c);
    z <= (a and b) or (not a and not b);
end;
```

Solution: The circuit has three inputs, A, B, C , and two outputs, Y, Z . Each output is defined by

$$Y = ABC + AB\bar{C} + A\bar{B}C$$
$$Z = AB + \bar{A}\bar{B}$$

We can simplify Y to:

$$\begin{aligned} Y &= AB\bar{C} + ABC + A\bar{B}C \\ &= AB\bar{C} + ABC + ABC + A\bar{B}C \\ &= AB + AC \\ &= A(B + C) \end{aligned}$$

The sketch of the circuit is in Figure 1. The circuit synthesized by Quartus II is in Figure 2.

Exercise 4.2. Sketch a schematic of the circuit described by the following HDL code. Simplify the schematic so that it shows a minimum number of gates.

 


Figure 1: Schematic sketch for Exercise 4-1

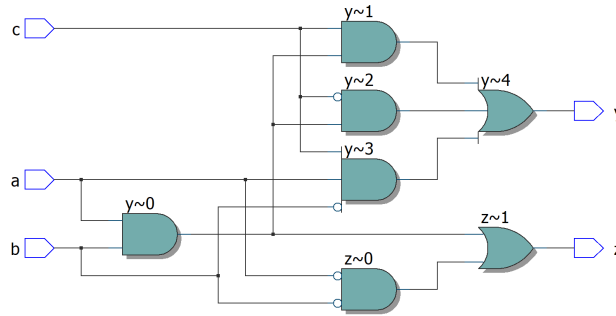


Figure 2: Synthesized Circuit by Quartus II for Exercise 4-1.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exercise2 is
    port(a: in STD_LOGIC_VECTOR(3 downto 0);
          y: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of exercise2 is
begin
    process(all) begin
        if a(0) then y <= "11";
        elsif a(1) then y <= "10";
        elsif a(2) then y <= "01";
        elsif a(3) then y <= "00";
        else
            y <= a(1 downto 0);
        end if;
    end process;
end;

```

Solution: Note that the input is $A_{3:0}$ and the output is $Y_{1:0}$. Then $Y_1 = A_0 + A_1$ and $Y_0 = A_0 + A_2\bar{A}_1$. The sketch of the circuit is in Figure 3. The circuit synthesized by Quartus II is in Figure 2.

Exercise 4.3. Write an HDL module that computes a four-input XOR function. The input is $a_{3:0}$ and the output is y .

 


Figure 3: Schematic sketch for Exercise 4-2

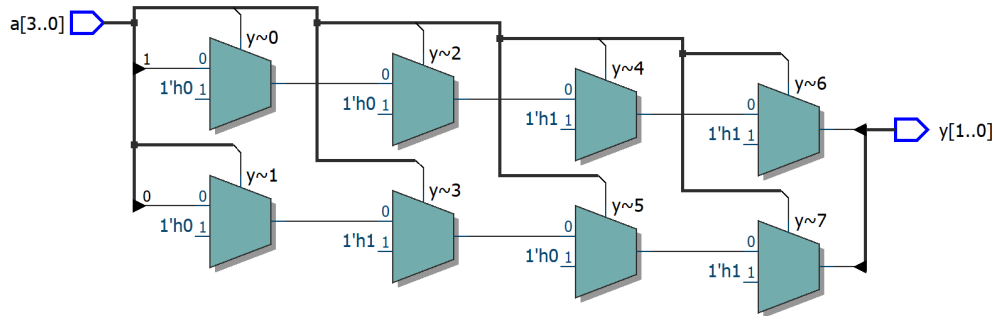


Figure 4: Synthesized Circuit by Quartus II for Exercise 4-2.

Solution: See the following listing, which can be found at `./hdl/03-04-xor4/xor4.vhd`:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

-- Exercise 4-3: Four-input XOR
entity xor4 is
    port(a: in STD_LOGIC_VECTOR(3 downto 0);
          y: out STD_LOGIC);
end;

architecture synth of xor4 is
begin
    y <= a(3) xor a(2) xor a(1) xor a(0);
end;

```

Exercise 4.4. Write a self-checking testbench for Exercise 4.3. Create a test vector file containing all 16 cases. Simulate the circuit and show that it works. Introduce an error in the test vector file and show that the testbench reports a mismatch.

Solution: The 16 cases are given in `./hdl/03-04-xor4/testvectors.txt`, available in the following listing:

```

0000_0

```

```
0001_1
0010_1
0011_0
0100_1
0101_0
0110_0
0111_1
1000_1
1001_0
1010_0
1011_1
1100_0
1101_1
1110_1
1111_0
```

The self-checking testbench is available in `./hdl/03_04/tb_xor4.vhd.`, which is a light modification of HDL Example 4.39. Specifically, it changes the file path to `../testvectors.txt`, and the component used from `sillyfunction` to `xor4`:

-- 4.39: testbench example 3, adapted for Exercise 4-4

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_TEXTIO.ALL; use STD.TEXTIO.all;

entity tb_xor4 is -- no inputs or outputs
end;

architecture sim of tb_xor4 is
  component xor4
    port(a: in STD_LOGIC_VECTOR(3 downto 0);
         y: out STD_LOGIC);
  end component;
  signal a: STD_LOGIC_VECTOR(3 downto 0);
  signal y: STD_LOGIC;
  signal y_expected: STD_LOGIC;
  signal clk, reset: STD_LOGIC;
begin
  -- instantiate device under test
  dut: xor4 port map(a, y);

  -- generate clock
  process begin
    clk <= '1'; wait for 5 ns;
    clk <= '0'; wait for 5 ns;
  end process;

  -- at start of test, pulse reset
```

```

process begin
    reset <= '1'; wait for 22 ns; reset <= '0';
    wait;
end process;

-- run tests
process is
    file tv: text;
    variable L: line;
    variable vector_in: std_logic_vector(3 downto 0);
    variable dummy: character;
    variable vector_out: std_logic;
    variable vectornum: integer := 0;
    variable errors: integer := 0;
begin
    FILE_OPEN(tv, "../testvectors.txt", READ_MODE);
    while not endfile(tv) loop

        -- change vectors on rising edge
        wait until rising_edge(clk);

        -- read the next line of testvectors and split into pieces
        readline(tv, L);
        read(L, vector_in);
        read(L, dummy); -- skip over underscore
        read(L, vector_out);
        a <= vector_in(3 downto 0) after 1 ns;
        y_expected <= vector_out after 1 ns;

        -- check results on falling edge
        wait until falling_edge(clk);

        report "just loaded stuff";
        if y /= y_expected then
            report "Error: y = " & std_logic'image(y);
            errors := errors + 1;
        end if;

        vectornum := vectornum + 1;
    end loop;

    -- summarize results at end of simulation
    if (errors = 0) then
        report "NO ERRORS -- " &
            integer'image(vectornum) &
            " tests completed successfully."
            severity failure;
    end if;
end process;

```

```

else
    report integer'image(vectornum) &
        " tests completed, errors = " &
        integer'image(errors)
        severity failure;
end if;
end process;
end;

```

By modifying the last entry in the `./hdl/03-04-xor4/testvectors.txt` so that it says `1111_1` instead, an error is reported, since the 4-input XOR gate should output 0 if there is an even number of 1s or all 0s, but the modified vector expects a 1.

Exercise 4.5. Write an HDL module called `minority`. It receives three inputs `a`, `b`, and `c`. It produces one output, `y`, that is TRUE if at least two of the inputs are FALSE.

Solution: The truth table for the Boolean function is below:

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

From the table we are able to identify the minterms and write

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

Though we could reduce the equation via Karnaugh maps, we let the HDL program handle the reduction. The listing is below:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity minority is
    port(a, b, c: in STD_LOGIC;
         y:      out STD_LOGIC);
end;

architecture synth of minority is
begin
    y <= (not a and not b and not c) or
        (not a and not b and c) or
        (not a and b and not c) or
        (a and not b and not c);
end;

```

 


Figure 5: Synthesized circuit for `minority` module in Exercise 4.5

The synthesized circuit is given in Figure 5. The truth table also forms the basis for the test vectors used in the test bench:

```

000_1
001_1
010_1
011_0
100_1
101_0
110_0
111_0

```

Using a self-checking testbench adapted from HDL Example 4.39, the simulation is successful, so the module correctly models the boolean function.

Exercise 4.6. Write an HDL module for a hexadecimal seven-segment display decoder. The decoder should handle the digits A, B, C, D, E and F, as well as 0-9.

Solution: Figure 6 and Figure 7 show the images from Chapter 2 for this circuit. Figure 8 shows the letters used in hexadecimal using seven segments. Notice that it uses lowercase *b* and *d*, since their uppercase versions would be confused with 8 and 0, respectively. The truth table is

 


Figure 6: Seven Segment Display Decoder Circuit

 


Figure 7: Seven Segment Display Digits

 


Figure 8: Seven Segment Display Hex Letters

$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
1010	1	1	1	0	1	1	1
1011	0	0	1	1	1	1	1
1100	1	0	0	1	1	1	0
1101	0	1	1	1	1	0	1
1110	1	0	0	1	1	1	1
1111	1	0	0	0	1	1	1

It is not necessary to create Boolean equations and write out the minterms. The following code listing shows the implementation:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity seven_segment_hex_decoder is
    port(data:    in  STD_LOGIC_VECTOR(3 downto 0);
          segments: out STD_LOGIC_VECTOR(6 downto 0));
end;

architecture synth of seven_segment_hex_decoder is
begin
    process(all) begin
        case data is --
            abcdefg
            when X"0" => segments <= "1111110";
            when X"1" => segments <= "0110000";
            when X"2" => segments <= "1101101";
            when X"3" => segments <= "1111001";
            when X"4" => segments <= "0110011";
            when X"5" => segments <= "1011011";
            when X"6" => segments <= "1011111";
            when X"7" => segments <= "1110000";
            when X"8" => segments <= "1111111";
            when X"9" => segments <= "1110011";
            when X"A" => segments <= "1110111";
            when X"B" => segments <= "0011111";
            when X"C" => segments <= "1001110";
            when X"D" => segments <= "0111101";

```

```

        when X"E" => segments <= "1001111";
        when X"F" => segments <= "1000111";
        when others => segments <= "0000000";
    end case;
end process;
end;

```

Exercise 4.7. Write a self-checking testbench for Exercise 4.6. Create a test vector file containing all 16 cases. Simulate the circuit and show that it works. Introduce an error in the test vector file and show that the testbench reports a mismatch.

Solution: We can use the following vector file, `testvectors.txt`:

```

0000_1111110
0001_0110000
0010_1101101
0011_1111001
0100_0110011
0101_1011011
0110_1011111
0111_1110000
1000_1111111
1001_1110011
1010_1110111
1011_0011111
1100_1001110
1101_0111101
1110_1001111
1111_1000111

```

The code listing below, `06-seven-segment-hex-decoder/tb_seven_segment_hex_decoder.vhd` is the testbench module:

-- 4.39: testbench example 3, adapted for Exercise 4-4

```

library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_TEXTIO.ALL; use STD.TEXTIO.all;

entity tb_seven_segment_hex_decoder is -- no inputs or outputs
end;

architecture sim of tb_seven_segment_hex_decoder is
    component seven_segment_hex_decoder
        port(data:    in  STD_LOGIC_VECTOR(3 downto 0);
             segments: out STD_LOGIC_VECTOR(6 downto 0));
    end component;
    signal data: STD_LOGIC_VECTOR(3 downto 0);

```

```

signal segments: STD_LOGIC_VECTOR(6 downto 0);
signal y_expected: STD_LOGIC_VECTOR(6 downto 0);
signal match: STD_LOGIC;
signal clk, reset: STD_LOGIC;
begin
    -- instantiate device under test
    dut: seven_segment_hex_decoder port map(data, segments);

    -- generate clock
    process begin
        clk <= '1'; wait for 5 ns;
        clk <= '0'; wait for 5 ns;
    end process;

    -- at start of test, pulse reset
    process begin
        reset <= '1'; wait for 22 ns; reset <= '0';
        wait;
    end process;

    -- run tests
    process is
        file tv: text;
        variable L: line;
        variable vector_in: std_logic_vector(3 downto 0);
        variable dummy: character;
        variable vector_out: std_logic_vector(6 downto 0);
        variable vectornum: integer := 0;
        variable errors: integer := 0;
    begin
        FILE_OPEN(tv, "../testvectors.txt", READ_MODE);
        while not endfile(tv) loop

            -- change vectors on rising edge
            wait until rising_edge(clk);

            -- read the next line of testvectors and split into pieces
            readline(tv, L);
            read(L, vector_in);
            read(L, dummy); -- skip over underscore
            read(L, vector_out);
            data <= vector_in(3 downto 0) after 1 ns;
            y_expected <= vector_out(6 downto 0) after 1 ns;

            -- check results on falling edge
            wait until falling_edge(clk);
            if (segments /= vector_out) then

```

```

    report "Error: data = ";
    for i in 0 to data'length - 1 loop
        report std_logic'image(segments(i));
    end loop;
    errors := errors + 1;
end if;

    vectornum := vectornum + 1;
end loop;

-- summarize results at end of simulation
if (errors = 0) then
    report "NO ERRORS -- " &
        integer'image(vectornum) &
        " tests completed successfully."
    severity failure;
else
    report integer'image(vectornum) &
        " tests completed, errors = " &
        integer'image(errors)
    severity failure;
end if;
end process;
end;

```

Exercise 4.8. Write an 8:1 multiplexer module called `mux8` with inputs `s2:0`, `d0`, `d1`, `d2`, `d3`, `d4`, `d5`, `d6`, `d7`, and output `y`.

Solution: The following code listing implements `mux8` with generics, where the inputs and outputs are vectors of any given length.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux8 is
    generic (N: integer := 2);
    port(d0, d1, d2, d3, d4, d5, d6, d7: in STD_LOGIC_VECTOR(N-1 downto 0);
        s: in STD_LOGIC_VECTOR(2 downto 0);
        y: out STD_LOGIC_VECTOR(N-1 downto 0));
end;

architecture synth of mux8 is
begin
    process(all) begin
        case s is
            when "000" => y <= d0;
            when "001" => y <= d1;

```

```

    when "010" => y <= d2;
    when "011" => y <= d3;
    when "100" => y <= d4;
    when "101" => y <= d5;
    when "110" => y <= d6;
    when "111" => y <= d7;
    when others => y <= (others => '0');
end case;
end process;
end;

```

Exercise 4.9. Write a structural module to compute the logic function $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using multiplexer logic. Use the 8:1 multiplexer from Exercise 4.8.

Solution: Recall, as discussed in Section 2.8.1, that any 2^N -input multiplexer can be programmed to perform any N -input multiplexer. Since Y has 3 inputs, we can use an 8-input multiplexer, which is precisely `mux8` from the previous exercise. We begin by creating the boolean table:

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

It serves as the basis for the test vector file, as well as the HDL module, listed in `./hdl/09-structmodule/st`

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity structmodule is
    port (a, b, c: in STD_LOGIC;
          y:      out STD_LOGIC);
end;

architecture struct of structmodule is
    component mux8
        generic(N: integer := 2);
        port(d0, d1, d2, d3, d4, d5, d6, d7: in STD_LOGIC_VECTOR(N-1 downto 0);
              s: in STD_LOGIC_VECTOR(2 downto 0);
              y: out STD_LOGIC_VECTOR(N-1 downto 0));
    end component;
    signal mux_out: STD_LOGIC_VECTOR(0 downto 0);

```

```

begin
  mux8_1: mux8 generic map(1)
    port map("1", "0", "0", "1", "1", "1", "0", "0", (a, b, c),
      mux_out);
  y <= mux_out(0);
end;

```

Exercise 4.10. Repeat Exercise 4.9 using a 4:1 multiplexer and as many NOT gates as you need.

Solution: Section 2.8.1 mentions its possible to represent any N -input logic function with a 2^{N-1} input multiplexer. We eliminate C and express the output of $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ in terms of C :

A	B	Y
0	0	\bar{C}
0	1	C
1	0	1
1	1	0

The mux4 is given below in `./hdl/10-structmodulemux4/mux4.vhd`

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux4 is
  generic (N: integer := 2);
  port(d0, d1, d2, d3: in STD_LOGIC_VECTOR(N-1 downto 0);
    s: in STD_LOGIC_VECTOR(1 downto 0);
    y: out STD_LOGIC_VECTOR(N-1 downto 0));
end;

architecture synth of mux4 is
begin
  process(all) begin
    case s is
      when "00" => y <= d0;
      when "01" => y <= d1;
      when "10" => y <= d2;
      when "11" => y <= d3;
      when others => y <= (others => '0');
    end case;
  end process;
end;

```

The boolean function is implemented in the module in `./hdl/10-structmodulemux4/structmodule.vhd`

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity structmodule is
    port(a, b, c: in STD_LOGIC;
          y:      out STD_LOGIC);
end;

architecture synth of structmodule is
    component mux4
        generic(N: integer := 2);
        port (d0, d1, d2, d3: in STD_LOGIC_VECTOR(N-1 downto 0);
              s:      in STD_LOGIC_VECTOR(1 downto 0);
              y:      out STD_LOGIC_VECTOR(N-1 downto 0));
    end component;
    signal mux_out: STD_LOGIC_VECTOR(0 downto 0);
begin
    mux4_1: mux4 generic map(1)
        port map((0 => not C), (0 => C), "1", "0", (a, b), mux_out);
    y <= mux_out(0);
end;

```

Exercise 4.12. Write an HDL module for an eight-input priority circuit.

Solution: See the code listing for ./hdl/12-priority8/priority8.vhd below:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity priority8 is
    port(a: in STD_LOGIC_VECTOR(7 downto 0);
          y: out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of priority8 is
begin
    process(all) begin
        case? a is
            when "1-----" => y <= (0 => '1', others => '0');
            when "01-----" => y <= (1 => '0', others => '0');
            when "001-----" => y <= (2 => '0', others => '0');
            when "0001----" => y <= (3 => '0', others => '0');
            when "00001---" => y <= (4 => '0', others => '0');
            when "000001--" => y <= (5 => '0', others => '0');
            when "0000001-" => y <= (6 => '0', others => '0');
            when "00000001" => y <= (7 => '0', others => '0');
            when others      => y <= (others => '0');
        end case;
    end process;
end;

```

```

        end case?;
    end process;
end;

```

Exercise 4.13. Write an HDL module for a 2:4 decoder.

Solution: A 2-input 4-output decoder chooses one of its 4 outputs according to the given input combination. See the table below:

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

See the code listing for `./hdl/13-decoder2.4/decoder2.4.vhd`.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder2_4 is
    port(a: in STD_LOGIC_VECTOR(1 downto 0);
         y: out STD_LOGIC_VECTOR(3 downto 0));
end;

architecture synth of decoder2_4 is
begin
    process(all) begin
        case a is
            when "00" => y <= "0001";
            when "01" => y <= "0010";
            when "10" => y <= "0100";
            when "11" => y <= "1000";
            when others => y <= "XXXX";
        end case;
    end process;
end;

```

Exercise 4.14. Write an HDL module for a 6:64 decoder using three instances of the 2:4 decoders from Exercise 4.13 and a bunch of three-input AND gates.

Solution: Let the input be $D_{5:0}$, and split them into three 2-bit groups: $D_{5:4}$, $D_{3:2}$, and $D_{1:0}$. Each group will be fed into a separate decoder, each producing outputs $A_{3:0}$, $B_{3:0}$, and $C_{3:0}$ as follows:

$$\begin{aligned}
 D_{5:4} &\rightarrow A_{3:0} \\
 D_{3:2} &\rightarrow B_{3:0} \\
 D_{1:0} &\rightarrow C_{3:0}
 \end{aligned}$$

Then, we'll have 64 different three-input AND gates. Letting $0 \leq i, j, k \leq 3$, we'll have AND gate for all 64 combinations of $Y_m = A_i B_j C_k$, where $m = 16i + 4j + k$. For example, if $D_{5:0}$ is all zeroes, then $D_{5:4}, D_{3:2}, D_{1:0}$ are also all zeroes, so that $A_0 = B_0 = C_0 = 1$. Since $Y_0 = A_0 B_0 C_0$, it follows that Y_0 , as required. If, on the other hand, any bit is 1, then one of A_0, B_0 , or C_0 will be 0, so the output Y_0 becomes 0, as required. All other cases are justified similarly.

The following code listing, `./hdl/14-decoder6_64/decoder6_64.vhd`, uses `generate` to loop and create all combinations.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder6_64 is
    port(d: in STD_LOGIC_VECTOR(5 downto 0);
         y: out STD_LOGIC_VECTOR(63 downto 0));
end;

architecture synth of decoder6_64 is
    component decoder2_4
        port(a: in STD_LOGIC_VECTOR(1 downto 0);
             y: out STD_LOGIC_VECTOR(3 downto 0));
    end component;
    signal a: STD_LOGIC_VECTOR(3 downto 0);
    signal b: STD_LOGIC_VECTOR(3 downto 0);
    signal c: STD_LOGIC_VECTOR(3 downto 0);
begin
    dec2_4a: decoder2_4 port map(d(5 downto 4), a);
    dec2_4b: decoder2_4 port map(d(3 downto 2), b);
    dec2_4c: decoder2_4 port map(d(1 downto 0), c);
    gen: for i in 0 to 3 generate
        gen: for j in 0 to 3 generate
            gen: for k in 0 to 3 generate
                y((16 * i) + (4 * j) + k) <= a(i) and b(j) and c(k);
            end generate;
        end generate;
    end generate;
end;
```

The following code listing, `./hdl/14-decoder6_64/tb_decoder6_64.vhd` is a self-checking test bench that verifies it works

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

entity tb_decoder6_64 is -- no inputs
end;
```

 


Figure 9: Circuit from Exercise 2.26 for Exercise 4.16

```

architecture sim of tb_decoder6_64 is
  component decoder6_64
    port(d: in STD_LOGIC_VECTOR(5 downto 0);
         y: out STD_LOGIC_VECTOR(63 downto 0));
  end component;
  signal d: STD_LOGIC_VECTOR(5 downto 0);
  signal y, y_expected: STD_LOGIC_VECTOR(63 downto 0);
begin
  dut: decoder6_64 port map(d, y);
  process begin
    for i in 0 to 63 loop
      y_expected <= (i => '1', others => '0');
      d <= STD_LOGIC_VECTOR(to_unsigned(i, d'length)); wait for 5 ns;
      if y /= y_expected then
        report "Assertion error";
      end if;
    end loop;
    wait; -- wait forever;
  end process;
end;

```

Exercise 4.16. Write an HDL module that implements the circuit from Exercise 2.26. See Figure 04-16-circuit.

Solution: See code listing `./hdl/16-exercise2_26/exercise2_26.vhd`:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exercise2_26 is
  port(a, b, c, d, e: in STD_LOGIC;
       y           : out STD_LOGIC);
end;

architecture synth of exercise2_26 is
begin
  y <= not (

```

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

Figure 10: Truth table for Exercise 4.18

```

not (
    (not (a and b))
    and (not (c and d)))
and e
);
end;

```

Exercise 4.18. Write an HDL module that implements the logic from Exercise 2.28. Pay careful attention to how you handle don't cares. See Figure 10.

Solution: We can make it so that the input combinations that lead to don't cares yield 0. See code listing ./hdl/18-exercise2_28/exercise2_26.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exercise2_28 is
    port(v: in STD_LOGIC_VECTOR(3 downto 0);
         y: out STD_LOGIC);
end;

architecture synth of exercise2_28 is
begin
    process(all) begin
        case v is

```

```

    when "1000" => y <= '1';
    when "1011" => y <= '1';
    when "1100" => y <= '1';
    when "1101" => y <= '1';
    when "1111" => y <= '1';
    when others => y <= '0';
end case;
end process;
end;

```

Exercise 4.19. Write an HDL module that implements the functions from Exercise 2.35.

Solution: The specification is that we have an input $A_{3:0}$, representing the numbers 0 through 15. There are two outputs: P is TRUE if the number is prime, and D is true if the number is divisible by 3. The truth table below shows the function inputs and outputs:

A_3	A_2	A_1	A_0	P	D
0	0	0	0	0	1
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	1	0	1

See code listing `./hdl/19-exercise2_35/exercise2_35.vhd`:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exercise2_35 is
    port(a:  in  STD_LOGIC_VECTOR(3 downto 0);
          p, d: out STD_LOGIC);
end;

architecture synth of exercise2_35 is
begin
    process(all) begin

```

```

case a is
  when 4D"0" => p <= '0'; d <= '1';
  when 4D"1" => p <= '0'; d <= '0';
  when 4D"2" => p <= '1'; d <= '0';
  when 4D"3" => p <= '1'; d <= '1';
  when 4D"4" => p <= '0'; d <= '0';
  when 4D"5" => p <= '1'; d <= '0';
  when 4D"6" => p <= '0'; d <= '1';
  when 4D"7" => p <= '1'; d <= '0';
  when 4D"8" => p <= '0'; d <= '0';
  when 4D"9" => p <= '0'; d <= '1';
  when 4D"10" => p <= '0'; d <= '0';
  when 4D"11" => p <= '1'; d <= '0';
  when 4D"12" => p <= '0'; d <= '1';
  when 4D"13" => p <= '1'; d <= '0';
  when 4D"14" => p <= '0'; d <= '0';
  when 4D"15" => p <= '0'; d <= '1';
end case;
end process;
end;

```

Exercise 4.24. Sketch the state transition diagram for the FSM described by the following HDL code.

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fsm2 is
  port(clk, reset: in STD_LOGIC;
        a, b:      in STD_LOGIC;
        y:         out STD_LOGIC);
end;

architecture synth of fsm2 is
  type statetype is (S0, S1, S2, S3);
  signal state, nextstate: statetype;
begin
  process(clk, reset) begin
    if reset then state <= S0;
    elsif rising_edge(clk) then
      state <= nextstate;
    end if;
  end process;

  process(all) begin
    case state is
      when S0 => if (a xor b) then
        nextstate <= S1;

```

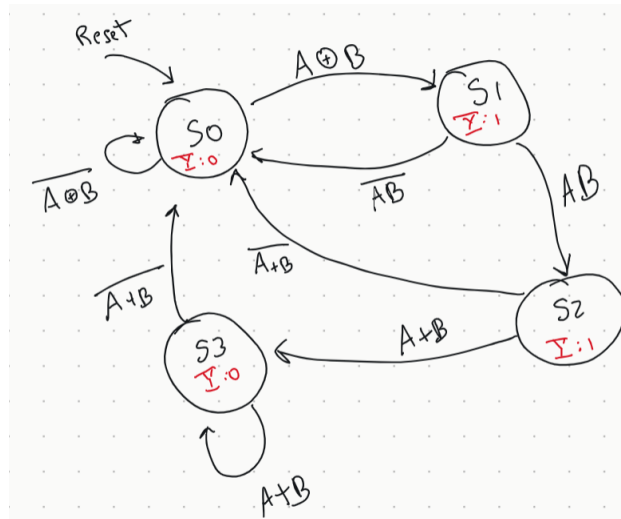


Figure 11: State Transition Diagram for Exercise 4.24

```

        else nextstate <= S0;
        end if;
    when S1 => if (a and b) then
        nextstate <= S2;
    else nextstate <= S0;
    end if;
    when S2 => if (a or b) then
        nextstate <= S3;
    else nextstate <= S0;
    end if;
    when S3 => if (a or b) then
        nextstate <= S3;
    else nextstate <= S0;
    end if;
end process;

y <= '1' when((state = S1) or (state = S2))
      else '0';
end;
```

Solution: This is a Moore state machine. See Figure 11.

Exercise 4.25. Sketch the state transition diagram for the FSM described by the following HDL code. An FSM of this nature is used in a branch predictor on some microprocessors.

```

library IEEE; use IEEE.STD_LOGIC_1164.all;

entity fsm1 is
    port(clk, reset: in STD_LOGIC;
          taken, back: in STD_LOGIC;
```

```

        predicttaken: in STD_LOGIC);
end;

architecture synth of fsm1 is
    type statetype is (S0, S1, S2, S3, S4);
    signal state, nextstate: statetype;
begin
    process(clk, reset) begin
        if reset then state <= S2;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    process(all) begin
        case state is
            when S0 => if taken then
                            nextstate <= S1;
                        else nextstate <= S0;
                        end if;
            when S1 => if taken then
                            nextstate <= S2;
                        else nextstate <= S0;
                        end if;
            when S2 => if taken then
                            nextstate <= S3;
                        else nextstate <= S1;
                        end if;
            when S3 => if taken then
                            nextstate <= S4;
                        else nextstate <= S2;
                        end if;
            when S4 => if taken then
                            nextstate <= S4;
                        else nextstate <= S3;
                        end if;
            when others => nextstate <= S2;
        end case;
    end process;

    -- output logic
    predicttaken <= '1' when
        ((state = S4) or (state = S3) or
         (state = S2 and back = '1'))
end;

```

Solution: This is a Mealy state machine. See Figure 12.

 


Figure 12: State Transition Diagram for Exercise 4.25

Exercise 4.26. Write an HDL module for an SR latch.

Solution: See code listing ./hdl/26-sr_latch/sr_latch.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity sr_latch is
    port(s, r: in STD_LOGIC;
         q, notq: out STD_LOGIC);
end;

architecture synth of sr_latch is
    signal qn, notqn: STD_LOGIC;
begin
    -- output
    q <= qn;
    notq <= notqn;
    -- inner nodes
    process(all) begin
        if (s = '0' and r = '1') then qn <= '0'; notqn <= '1';
        elsif (s = '1' and r = '0') then qn <= '1'; notqn <= '0';
        elsif (s = '1' and r = '1') then qn <= '0'; notqn <= '0';
        end if;
    end process;
end;

```

Exercise 4.27. Write an HDL module for a *JK flip-flop*. The flip-flop has inputs *CLK*, *J*, and *K*, and output *Q*. On the rising edge of the clock, *Q* keeps its old value if *J* = *K* = 0. It sets *Q* to 1 if *J* = 1, resets *Q* to 0 if *K* = 1, and inverts *Q* if *J* = *K* = 1.

Solution: See code listing ./hdl/27-jk_ff/jk_ff.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity jk_ff is
  port(j, k: in STD_LOGIC;
        clk: in STD_LOGIC;
        q: out STD_LOGIC);
end;

architecture synth of jk_ff is
begin
  process(clk) begin
    if rising_edge(clk) then
      if j = '1' and k = '1' then q <= not q;
      elsif j = '1' and k = '0' then q <= '1';
      elsif j = '0' and k = '1' then q <= '0';
      end if;
    end if;
  end process;
end;

```

Exercise 4.29. Write an HDL module for the traffic light controller from Section 3.4.1.

Solution: See code listing ./hdl/29-traffic_light/traffic_light.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity traffic_light is
  port(ta, tb: in STD_LOGIC;
        clk, reset: in STD_LOGIC;
        la, lb: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of traffic_light is
  type statetype is (S0, S1, S2, S3);
  signal state, nextstate: statetype;
begin
  process(clk, reset) begin
    if reset then state <= S0;
    elsif rising_edge(clk) then
      state <= nextstate;
    end if;
  end process;

  -- green: 00, yellow: 01, red: 10
  process(all) begin

```

 


Figure 13: Factored Traffic Light State Machine Design for Exercise 4.30

```

case state is
  when S0 => if ta then nextstate <= S0;
              else      nextstate <= S1;
              end if;
  when S1 => nextstate <= S2;
  when S2 => if tb then nextstate <= S2;
              else      nextstate <= S3;
              end if;
  when S3 => nextstate <= S0;
  when others => nextstate <= S0;
end case;
end process;

process(all) begin
  case state is
    when S0 => la <= "00"; lb <= "10";
    when S1 => la <= "01"; lb <= "00";
    when S2 => la <= "10"; lb <= "00";
    when S3 => la <= "10"; lb <= "01";
  end case;
end process;
end;

```

Exercise 4.30. Write HDL modules for the factored parade mode traffic light controller from Example 3.8. The modules should be called `controller`, `mode`, and `lights`, and they should have the inputs and outputs shown in Figure 13. See the state transition diagram in Figure 14.

 


Figure 14: Factored Traffic Light State Transition Diagram for Exercise 4.30

Solution: The mode module is in listing ./hdl/30-traffic_fsm_factored/mode.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mode is
    port(p, r:      in  STD_LOGIC;
         clk, reset: in  STD_LOGIC;
         m:         out STD_LOGIC);
end;

architecture synth of mode is
    type statetype is (S0, S1);
    signal state, nextstate: statetype;
begin
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    process(all) begin
        case state is
            when S0 => if p then nextstate <= S1;
                       else nextstate <= S0;
                       end if;
            when S1 => if r then nextstate <= S0;
                       else nextstate <= S1;
                       end if;
        end case;
    end process;
end process;

```

```

    m <= '1' when (state = S1) else '0';
end;

```

```

:
    The lights module is in listing ./hdl/30-traffic_fsm_factored/lights.vhd:

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity lights is
    port(ta, tb, m: in STD_LOGIC;
         clk, reset: in STD_LOGIC;
         la, lb: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of lights is
    type statetype is (S0, S1, S2, S3);
    signal state, nextstate: statetype;
begin
    process(clk, reset) begin
        if reset then state <= S0;
        elsif rising_edge(clk) then
            state <= nextstate;
        end if;
    end process;

    process(all) begin
        case state is
            when S0 => if ta then nextstate <= S0;
                       else nextstate <= S1;
                       end if;
            when S1 => nextstate <= S2;
            when S2 => if (m or tb) then nextstate <= S2;
                       else nextstate <= S3;
                       end if;
            when S3 => nextstate <= S0;
        end case;
    end process;

    process(all) begin
        case state is -- green="00", yellow="01", red="10"
            when S0 => la <= "00"; lb <= "10";
            when S1 => la <= "01"; lb <= "10";
            when S2 => la <= "10"; lb <= "00";
            when S3 => la <= "10"; lb <= "01";
        end case;
    end process;
end;

```

```
end;
```

```
:
```

The controller module is in listing ./hdl/30-traffic_fsm_factored/controller.vhd:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity controller is
    port(p, r, ta, tb: in STD_LOGIC;
         clk, reset: in STD_LOGIC;
         la, lb: out STD_LOGIC_VECTOR(1 downto 0));
end;

architecture synth of controller is
    component lights
        port(ta, tb, m: in STD_LOGIC;
             clk, reset: in STD_LOGIC;
             la, lb: out STD_LOGIC_VECTOR(1 downto 0));
    end component;
    component mode
        port(p, r: in STD_LOGIC;
             clk, reset: in STD_LOGIC;
             m: out STD_LOGIC);
    end component;
    signal m: STD_LOGIC;
begin
    mode_fsm: mode port map(p, r, clk, reset, m);
    lights_fsm: lights port map(ta, tb, clk, reset, m);
end;
```

```
:
```

Exercise 4.31. Write an HDL describing the circuit in Figure ??.

Solution: See code listing ./hdl/31-exercise31/exercise31.vhd:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity exercise31 is
    port(a, b, c, d: in STD_LOGIC;
         clk: in STD_LOGIC;
         x, y: out STD_LOGIC);
end;

architecture synth of exercise31 is
    signal aa, bb, cc, dd, n2: STD_LOGIC;
begin
```

```
process(clk) begin
  if rising_edge(clk) then
    aa <= a;
    bb <= b;
    cc <= c;
    dd <= d;
    x <= n2;
    y <= not (n2 or dd);
  end if;
end process;
n2 <= (aa and bb) or cc;
end;
```
